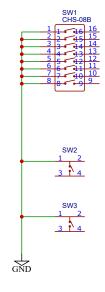
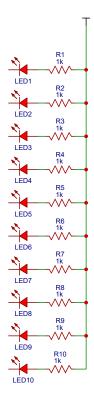


— DEPARTMENT OF —
ELECTRICAL & COMPUTER
ENGINEERING







NOTES:

1) AVOID PORT 0 (BITS 0 AND 1 WILL BE USED FOR THE SERIAL PORT) AND AVOID PORTS 4, 6 AND 7 (THESE WILL BE USED FOR BUS EXPANSION LATER). MAKE THE LEDS TURN ON WHEN THE CORRESPONDING PORT LINES ARE LOW.

TITLE: Lab02 Input/Output REV: 1.0

Company: ECE3710 Sheet: 1/1
Date: 2023-01-23 Drawn By: Jacob Watts